

**Indian Maritime University**  
(A Central University, Govt. Of India)  
**B. Tech. (Marine Engineering)**

Semester II

End Semester Examination June 2022

**Basic Electronics**  
**(UG11T4203)**

**Time: 3 Hours**  
**Date: 22/06/2022**

**Max Marks: 70**  
**Pass Marks: 35**

**Part – A (Compulsory)**

**Q.1 Answer the following (10x2=20 Marks)**

- (I) The electrical resistance of the depletion layer is large because
- a) It has no charge carriers
  - b) It has a large number of charge carriers
  - c) It contains electrons as charge carriers
  - d) It has holes as charge carriers
- (II) The doped region in a transistor is
- a) Emitter and Collector
  - b) Emitter and Base
  - c) Collector and Base
  - d) Emitter, Collector and Base
- (III) What is the full form of SCR?
- a) Silicon controlled rectifier
  - b) Silicate controlled rectifier
  - c) Silicon controlled rectification
  - d) Silicon controlling rectification
- (IV) Which gate will a NAND gate be equivalent to when two inputs of NAND gates are shorted?
- a) AND gate
  - b) OR gate
  - c) NAND gate
  - d) NOT gate
- (V) Which is the major functioning responsibility of the multiplexing combinational circuit?
- a) Decoding the binary information
  - b) Generation of all min terms in an output function with OR-gate
  - c) Generation of selected path between multiple sources and a single destination

- d) Encoding of binary information
- (VI) Which of the following is not a condition flag?  
a) Trap flag  
b) Auxiliary carry flag  
c) Parity flag  
d) Zero flag
- (VII) . A multivibrator is an electronic circuit used to implement  
\_\_\_\_\_  
a) Oscillator  
b) Timer  
c) Flip-flop  
d) All of the Mentioned
- (VIII) In an ideal op-amp, which is not true?  
a) Open loop voltage gain is infinite  
b) Input resistance is infinite  
c) Slew rate is infinite  
d) CMRR is zero
- (IX) . The \_\_\_\_\_ symbol is used to represent decision in flowchart.  
a) Circle  
b) Rectangle  
c) Diamond  
d) None of these
- (X) . Which of the following terminals does not belong to the MOSFET?  
a) Drain  
b) Gate  
c) Base  
d) Source

**Part – B (Compulsory)**  
**(5 x 2= 10 marks)**

**Q.2 Answer the following**

- (I) . What is the function of relay?
- (II) . What is a Flowchart?
- (III). Define ripple factor.
- (IV) Define slew rate in OP-AMP.
- (V). Why CE configuration is commonly used?

**Part C – Answer any 5 out of 7 Questions**  
**(05 X 10 Marks)**

- Q.3a)** An Astable 555 Oscillator is constructed using the following components,  $R_1 = 1k\Omega$ ,  $R_2 = 2k\Omega$  and capacitor  $C = 10\mu F$ . Calculate the output frequency from the 555 oscillator and the duty cycle of the output waveform. (5 M)
- Q.3b)** Define drain resistance ( $r_d$ ), transconductance ( $g_m$ ), and amplification factor ( $\mu$ ) of a FET and derive relation among them. (5 M)
- Q.4a)** Explain the addressing modes of 8085 microprocessor with examples. (5 M)
- Q.4b)** Write a program of 8085 microprocessor to add the contents of memory locations 4000H and 4001H and place the result in memory location 4002H. (5 M)
- Q.5a)** Draw block diagram of PLC and explain each block in brief. (5 M)
- Q.5b)** Draw and explain one-bit half adder. (5 M)
- Q.6a)** Simplify the following using K map.  $f(A, B, C, D) = \sum m(7,8,9) + \sum d(10,11,12,13,14,15)$  (5 M)
- Q.6b)** Draw the circuit diagram of an OP-AMP summing circuit to provide  $V_{out} = -V_1 + 3V_2 - 5V_3$  where  $V_1$ ,  $V_2$  and  $V_3$  are positive inputs. (5 M)
- Q.7a)** Draw and explain V/I characteristic of SCR. (5 M)
- Q.7b)** Explain Integrated Automation Control and Monitoring System (IACMS) with block diagram. (5 M)
- Q.8a)** Explain Block diagram, operation of single slope type ADC. (5 M)
- Q.8b)** Explain the principle and working of Frequency meter. (5 M)
- Q.9a)** What is Clamper? Draw diagram and explain working of negative clamper? (5 M)
- Q.9b)** Draw the typical frequency response curve of a CE amplifier. How do you find out the bandwidth of amplifier? (5 M)