

Indian Maritime University
(A Central University, Govt. of India)
B.Sc. (Nautical Science)
END SEMESTER EXAMINATIONS- JUNE/JULY 2019
SEMESTER-III
NAUTICAL ELECTRONICS PAPER-I
UG21T2304

Date: 02.07.2019

Maximum marks: 70

Duration: 3 Hrs

Pass Marks: 35

Attempt any **SEVEN** questions . All carry equal marks. (7x10=70)

- 1.(a) Sketch series RLC circuit connected to A.C source and derive equation for current and resonance frequency. (5)
- (b) A circuit consists of a capacitor of 100 pF connected in series with coil of resistance of 5 Ω and inductor of 100 μ H. Calculate resonance frequency and Q factor. (5)
- 2.(a) Define the terms active power, reactive power and power factor in a.c circuit. (5)
- (b) A coil having L = 0.14 H and R = 9.43 Ω connected across 50 Hz 135 V supply. Determine X_L , Z and I. (5)
- 3.(a) What is need for modulation in communication system. (5)
- (b) Compare amplitude modulation and frequency modulation. (5)
- 4.(a) Explain with the help of waveforms the process of amplitude modulation. (5)
- (b) Define modulation index. Modulated carrier wave has maximum and minimum amplitude of 750 mV and 250 mV. Calculate the percentage of modulation. (5)
- 5.(a) Explain the process of demodulation using diode detector circuit for Amplitude Modulated signal. (5)
- (b) The carrier frequency in a F.M modulator is 1000 KHz. If the modulation frequency is 15 KHz, what are the first three upper side band and lower side band frequencies. (5)

- 6.(a) Show the parallel RLC circuit connected to a.c source and its current waveforms. Also state the resonant frequency of the circuit. (5)
- (b) Parallel RLC circuit consisting of 200 pF capacitor, inductor of 200 μ H and resistance of 5 Ω is connected across 1.0 V, 800 KHz signal source. Determine resonant frequency and Q value. (5)
- 7.(a) A frequency modulated voltage wave is given by the equation $e = 12 \cos (6 \times 10^8 t + 5 \sin 1250 t)$, determine carrier frequency, signal frequency and modulation index. (5)
- (b) Calculate the modulation index for Frequency modulated wave where the maximum frequency deviation is 50 KHz and the modulation frequency is 5 KHz. (5)
8. (a) Discuss the classification of amplifiers. (5)
- (b) Describe the circuit of push-pull amplifier. (5)
9. (a) State the main characteristics of series RLC circuit. (5)
- (b) Describe a transistor circuit of simple A.M modulator. (5)
