

Indian Maritime University
(A Central University, Govt. Of India)
B. Tech. (Marine Engineering)

Semester IV

End Semester Examination June 2022

Digital Electronics and PLC
(UG11T3402)

Time: 3 Hours
Date: 03/06/2022

Max Marks: 70
Pass Marks: 35

Part – A (Compulsory)

Q.1 Answer the following

(10x1=10 Marks)

- (I) What will be the output from a JK flip-flop if $J=K = 1$ and the clock is valid?
- No change
 - Toggle between 0 and 1
 - 0
 - 1
- (II) What determines the output from the combinational logic circuit in Digital Electronics?
- Input signals from the past condition
 - Input signals at the present moment
 - Input signals from both past and present
 - Input signals expected in future
- (III) Which of these sets of logic gates are known as universal gates?
- XOR, NAND, OR
 - OR, NOT, XOR
 - NOR, NAND, XNOR
 - NOR, NAND
- (IV) What is SCADA?
- Software
 - Process
 - System
 - Hardware
- (V) Find out the resolution of 8-bit DAC/ADC?
- 562
 - 625
 - 256
 - 265

- (VI) Which of the following is not a condition flag?
a) Trap flag
b) Auxiliary carry flag
c) Parity flag
d) Zero flag
- (VII) . Which of the logic family uses FET as its switching element?
a) TTL
b) Diode logic
c) CMOS
d) None of the above
- (VIII). CRO is used for measurement of _____
a) AC as well as DC current
b) AC current only
c) DC current only
d) AC power only
- (IX) . Which of the following memories must be refreshed many times per second?
a) EPROM
b) ROM
c) Static RAM
d) Dynamic RAM
- (X). _____ is an 8-bit register for 8085 microprocessors.
a) Stack pointer
b) Accumulator
c) Program counter
d) Memory pointer

Part – B (Compulsory)
(5 x 2= 10 marks)

Q.2 Answer the following

- (I). What is the function of carry flag?
- (II). What is a Q meter?
- (III). write two applications of flip flop.
- (IV). Simplify using Boolean algebra $AB + A(B+C) + B(B+C)$
- (V). Define: fan in of a Gate.

Part C – Answer any 5 out of 7 Questions
(05 X 10 Marks)

- Q.3a)** Give advantages of CMOS IC family. (5 M)
- Q.3b)** Define Resolution, Accuracy of a Digital to Analog Convertor. (5 M)
- Q.4a)** Explain the addressing modes of 8085 microprocessor with examples. (5 M)
- Q.4b)** Write a program of 8085 microprocessor to add the contents of memory locations 8000H and 8001H and place the result in memory location 8002H. (5 M)
- Q.5a)** Draw block diagram of PLC and explain each block in brief. (5 M)
- Q.5b)** Draw and explain one-bit half adder. (5 M)
- Q.6a)** Simplify the following using K map. $f(A, B, C, D) = \sum m(7,8,9) + \sum d(10,11,12,13,14,15)$ (5 M)
- Q.6b)** Compare S-RAM and D-RAM. (5 M)
- Q.7a)** Draw and explain architecture of SCADA (5 M)
- Q.7b)** Construct 8:1 multiplexer from 4:1 multiplexer (5 M)
- Q.8a)** Explain Block diagram, operation of single slope type ADC. (5 M)
- Q.8b)** Explain the principle and working of Frequency meter. (5 M)
- Q.9a)** Draw and explain flag register of 8085 microprocessor. (5 M)
- Q.9b)** Design 3 bit binary to gray code converter (5 M)