

INDIAN MARITIME UNIVERSITY
(A Central University, Government of India)

May/June End Semester Examinations
B.Sc. (Nautical Science) Fourth Semester
(AY 2013-14 to 2015- 16 batches only)

Nautical Electronics – IV (UG21T2405)

Date : 10.06.2017

Maximum Marks: 70


Time: 3 Hrs

Pass Marks : 35

Note: Answer any seven of the following.

All questions carry equal marks. (7 x 10 marks = 70 marks)

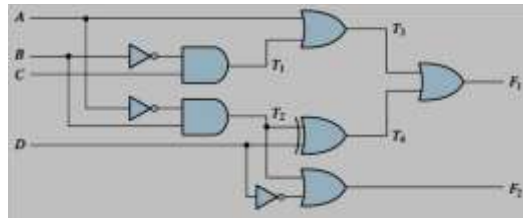1. a) What is called universal gates? Implement AND, OR and NOT Gates by using NAND Gate. (5)
- b) State and verify De Morgan's theorems. (5)
2. a) Using Boolean techniques, simplify $Y = AB + A(B + C) + B(B + C)$. (5)
- b) Explain Full adder circuit with truth table and logic diagram. (5)
3. Consider the combinational circuit shown below, derive the Boolean expressions for T_1 through T_4 . Evaluate the outputs F_1 and F_2 as a function of the four inputs. (5 + 5)



4. a) Draw the internal structure of IC 555, explain the function of each pins. (5)
- b) Explain NAND gate as clock pulse generator. (5)

5. a) Explain RS latch with NOR Gates, with neat sketch and truth table. (5)
- b) Draw a logic diagram for JK flip flop, from truth table explain what is called toggle state. (5)
6. a) With neat sketch explain the working principle of 3 – bit ripple counter. (5)
- b) What is called non binary counter? Draw a neat sketch of 4 – bit decade counter and derive the truth table. (5)
7. a) Implement the following Boolean function with a multiplexer.
 $F(A, B, C, D) = \Sigma(0, 2, 5, 8, 10, 14)$ (5)
- b) Implement a full adder with two 4×1 multiplexers. (5)
8. Draw pin diagram and an internal architecture of 8085 microprocessor. (10)
9. a) Define Interrupts in 8085 processor and list the types. (5)
- b) Discuss programming model of 8085 processor. (5)
