

**INDIAN MARITIME UNIVERSITY**  
(A Central University, Government of India)  
**End Semester Examination Dec 2019/Jan 2020**  
**B.Sc. (Nautical Science)**  
**Semester -II**  
**UG21T3202 - Applied Physics & electricity**

---

**Date: 03.01.2019**  
**Time: 3 Hours**

**Max Marks: 70**  
**Pass Marks: 35**

---

**PART-A**

**(Compulsory question)**

**(5 × 2 = 10)**

1. a) Define coupling coefficient.
- b) Define Resonant frequency.
- c) Define Quality factor of a coil.
- d) State Kirchhoff current and voltage law.
- e) Define the term Precision.

**PART-B**

**(Attempt any six questions out of eight)**

**(6 × 10 = 60)**

2. a) State and explain the faradays law of electromagnetic induction. (5)
- b) Magnetic field through a coil having 200 turns and cross sectional area  $0.04\text{m}^2$  changes from  $0.1\text{wbm}^{-2}$  to  $0.04\text{wbm}^{-2}$  in  $0.02\text{S}$ . find the induced emf. (5)
3. a) What do you understand by the terms power factor, active power and Reactive power. (5)
- b) A resistance of  $20\Omega$  and an inductance of  $0.2\text{H}$  and a capacitance of  $100\mu\text{F}$  are connected in series across  $220\text{V}$ ,  $50\text{Hz}$  main supply. Determine the following a) impedance b) current c) voltage across R, L and C. (5)
4. a) Explain with neat sketch, the desauty bridge network and arrive at the

equations. (5)

b) The four arms of a Hays ac bridge are arranged as follows. (5)

AB is a coil of unknown impedance.


BC is a non-reactive resistor of  $1000\Omega$

CD is a non-reactive resistor of  $833\Omega$  in series with a standard capacitor of  $0.38\mu\text{F}$

DA is a non-reactive resistor of  $16,800\Omega$ .if the supply frequency is  $50\text{Hz}$ .determine the inductance and the resistance at the balance condition.

5. a) State and explain Thevenins Theorem. (5)

b) Solve using Norton's Theorem. (5)

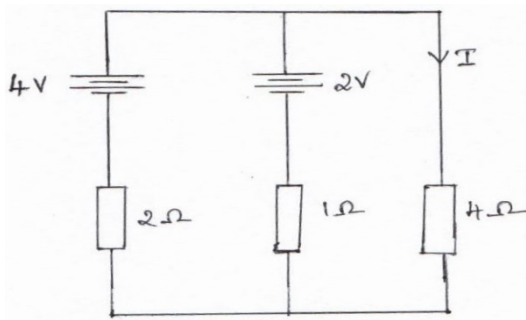

6. a) Explain with neat diagram, principle, construction and working of DC generator. (5)

b) An a.c generator consists of a coil of 10,000 turns and of area  $100\text{ cm}^2$ .The coil rotates at an angular speed of 140 rpm in a uniform magnetic field of  $3.6 \times 10^{-2}$  Find the maximum value of the emf induced. (5)

7. a) What is thermistor and how it is applied as a heat sensor. (5)

b) Explain the Series and Shunt type DC motors. (5)

8. A four arm bridge ABCD consists of

AB-fixed resistor  $R_1$

BC-a variable resistor  $R_2$  in series with a variable capacitor  $C_2$ .

CD- a fixed resistor  $R_3$ .

DA –a coil of unknown resistance  $R$  and inductance  $L$ .

Determine the values of  $R$  and  $L$ , if at balance,  $R_1 = 1\text{K}\Omega$ ,  $R_2 = 2.4\text{K}\Omega$ ,  
 $C_2 = 4000\text{ pf}$ ,  $R_3 = 1\text{K}\Omega$

And the supply frequency is 1.6 kHz. (10)

9. Write short notes on any two. (2X5=10)

- a) Millman Theorem.
- b) Transducer.
- c) Heating effect of electric current.
- d) Venturitube.

\* \* \* \* \*